

Tuesday 17th November 2020

Science M3 WALT: associate the brightness of a lamp, or the volume of a buzzer with the number and voltage of cells used in the circuit.

Science M3 SCI WALT: report findings from enquiries, including oral and written explanations of results, explanations, involving causal relationships, and conclusions.

<p><b>Basic</b></p> <p>Observe and describe the effect of changing the number and voltage of cells used in a simple circuit.</p>	<p><b>Advancing</b></p> <p>Experiment with, explain and demonstrate the pattern between the voltage of cells and the brightness of a bulb.</p>	<p><b>Deep</b></p> <p>Suggest why a bulb or buzzer may stop working when the voltage is increased.</p>
--	--	--

1. Do you recognise these objects?  
 2. Which is an odd one out?  
 3. How are they the same and how are they different?

a) coin cell battery  
 b) standard battery  
 c) Duracell battery

1. These objects are all types of batteries:  
 a = watch battery  
 b = car battery  
 c = normal electronics battery

2. I think b is the odd one out as it powers something much larger than the others also it is the only one that recharges.

3. They are all similar as they are all batteries. They are different because they all power different sized objects.

Recap....

Draw a line to match the component to its symbol.

